

## EENG 5560 HW 2

Name: \*Hari Krishna \*

## Table of Contents

Block diagram for 2x2 reconfigurable computing architecture .....	3
Design\Algorithm ex: .....	4
Generated RTL Block Diagram\Schematic .....	5
Results .....	5
Waveforms .....	5
Table .....	6

## Block diagram for 2x2 reconfigurable computing architecture

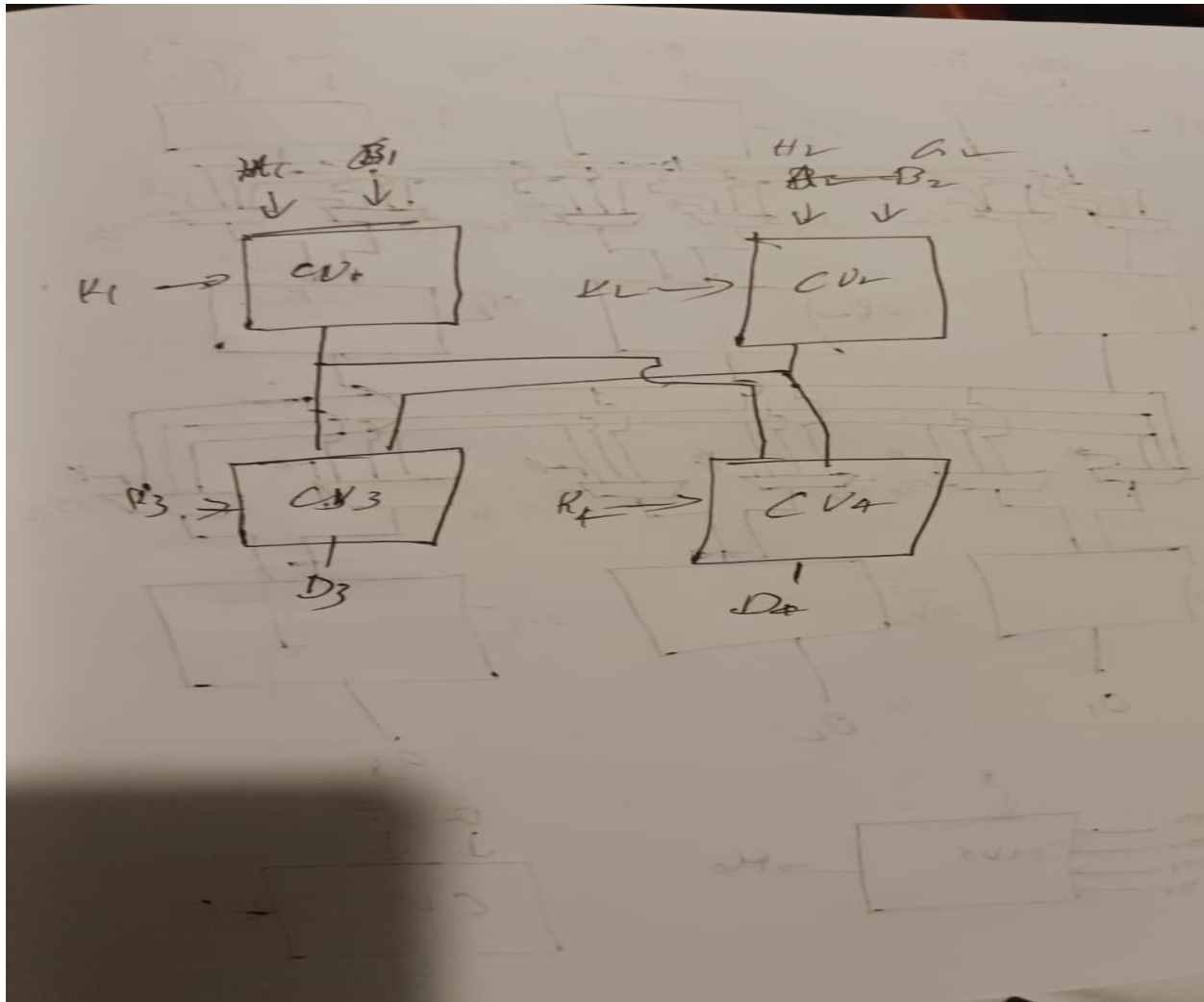


Figure 2x2 reconfigurable computing

- Overall Component: 2x2 reconfigurable computing architecture
- Overall ports:
  - Inputs: H1, H2, G1, G2 – input to computational unit
    - K1, K2, K3, K4 – Selection lines for computational unit.
  - Outputs:
    - D3, D4 – Output.
- Sub Component:
  - Computation unit:
    - H, G – input
    - K – Selection input
    - D – Output

- Necessary intermediate signals:
  - D1,D2.

### Design\Algorithm ex:

 


Figure 2– 2x2 reconfigurable computing

- Overall Component:
- Overall ports:
  - Inputs:
    - H1: 4 bits
    - H2: 4 bits
    - G1: 4 bits
    - G2: 4 bits
    - K1, K2, K3, K4: 3bits -> select line input
  - Outputs:
    - D3: 4 bit -> output
    - D4: 4 bit -> Output

## Generated RTL Block Diagram\Schematic

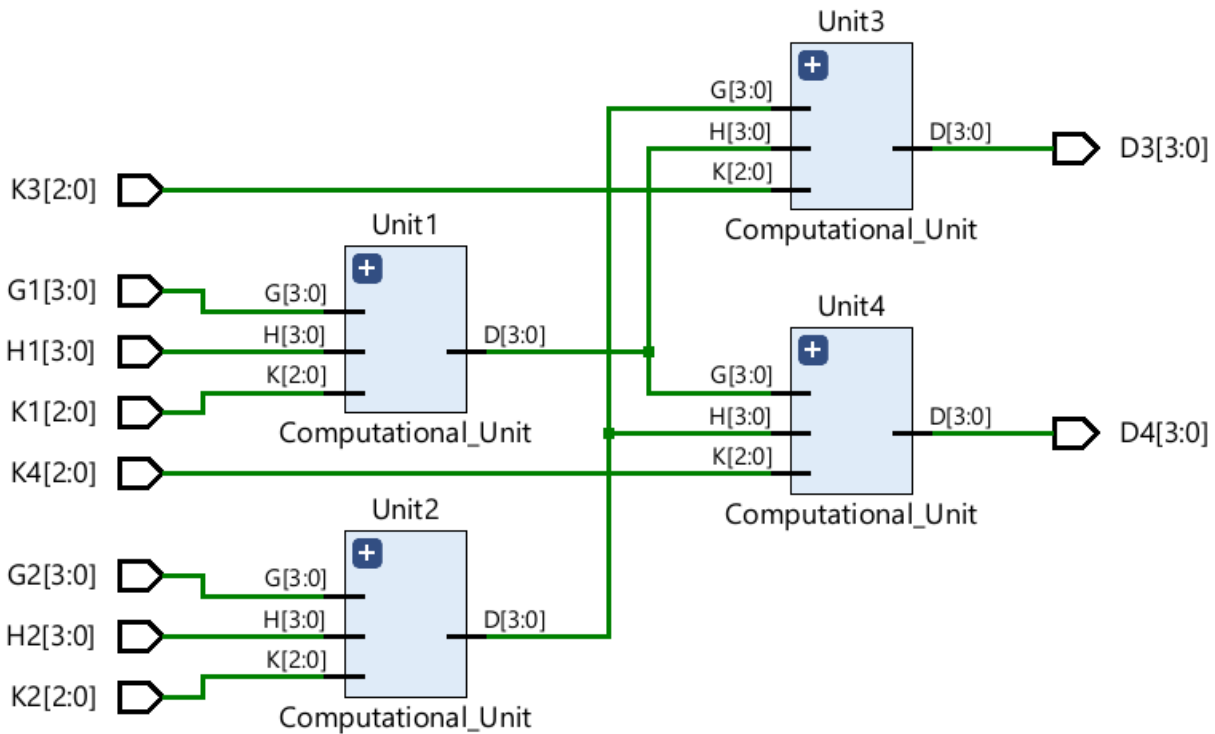


Figure 1 - generated RTL schematic.

## Results

### Waveforms

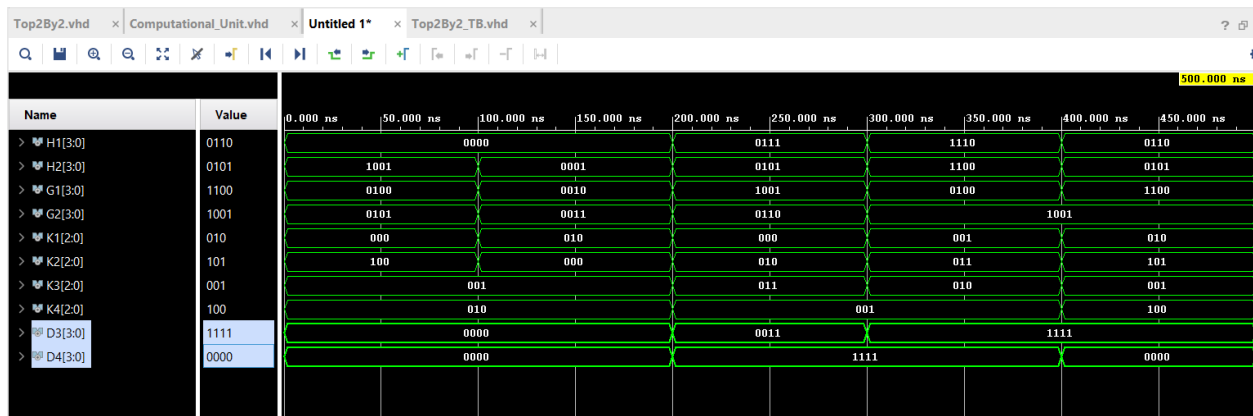


Figure 2 - Waveforms

**Table**

	calculations										waveforms	
	H1	H2	G1	G2	K1	K2	K3	K4	D1	D2	D1	D2
Test case 1:	0000	0011	0000	0100	000	001	010	010	0000	0000	0000	0000
Test case 2:	0111	0101	1001	0110	000	010	011	010	0000	0011	0000	1111